

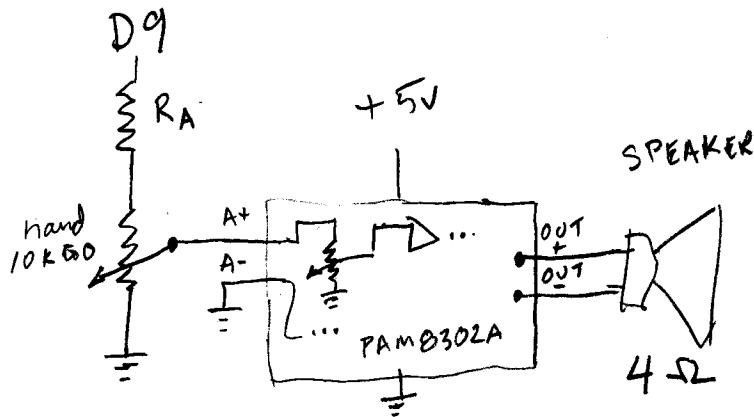


Circuit A

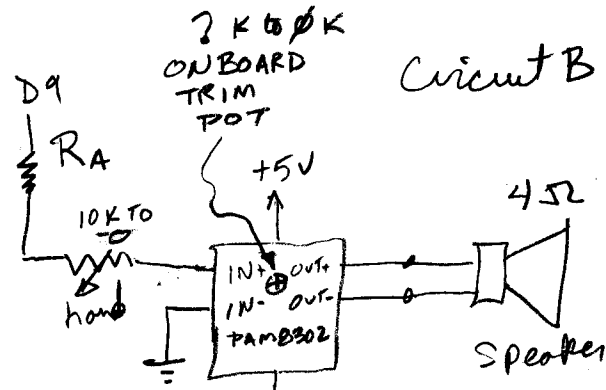

$$R_A = 2000 \Omega$$

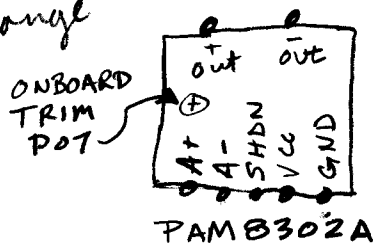work great -  
use Trim POT to set max vol  
use hand POT to control  
from 0 to max vol over  
full range



worked loudly,  $R_A = 2K$ .  
had to turn up TRIM POT.  
0 to 10K POT had small  
effect.

$R_A = 10K$ , TRIM POT = 0K  
TOO LOUD, hand POT = 10K  
TRIM POT higher,  
hand POT has small effect.

ON BOARD TRIM POT APPEARS  
TO BE 9K OHMS, and is  
in a DIVIDER POT CONF  
Tapped on  
wiper


used a regulated +5V supply  
to test all circuits  
also used unregulated supply  
on Circuit A - worked OK

$$I = E/R = 5/220 = 23\text{ma}$$

$$= 5/2000 = 2.5\text{ma}$$

$$= 5/10000 = 0.5\text{ma}$$

Circuit C

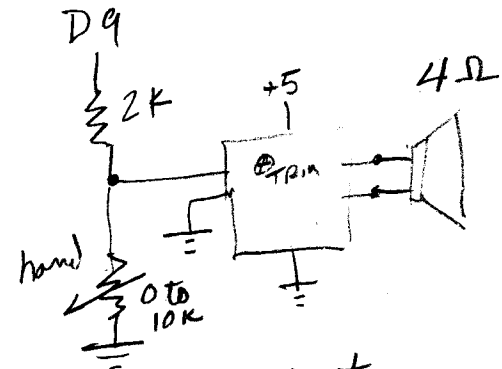

worked but  
control was poor  
almost full vol at  
about half of hand  
pot range -  
used trim pot  
for max vol.

ALTERNATE POT  
CIRCUITS  
C.SPINDLER 1-24-2020

DWG NO.

CFS-1-24-2020-B